



5V tolerant IO

MCD application



Background


2

- STM32s embed the 5V tolerant pads.
- Those pad can communicate 5V signaling, however it needs certain pre-caution and the external circuitry in some cases.



Ordinary CMOS IO structure

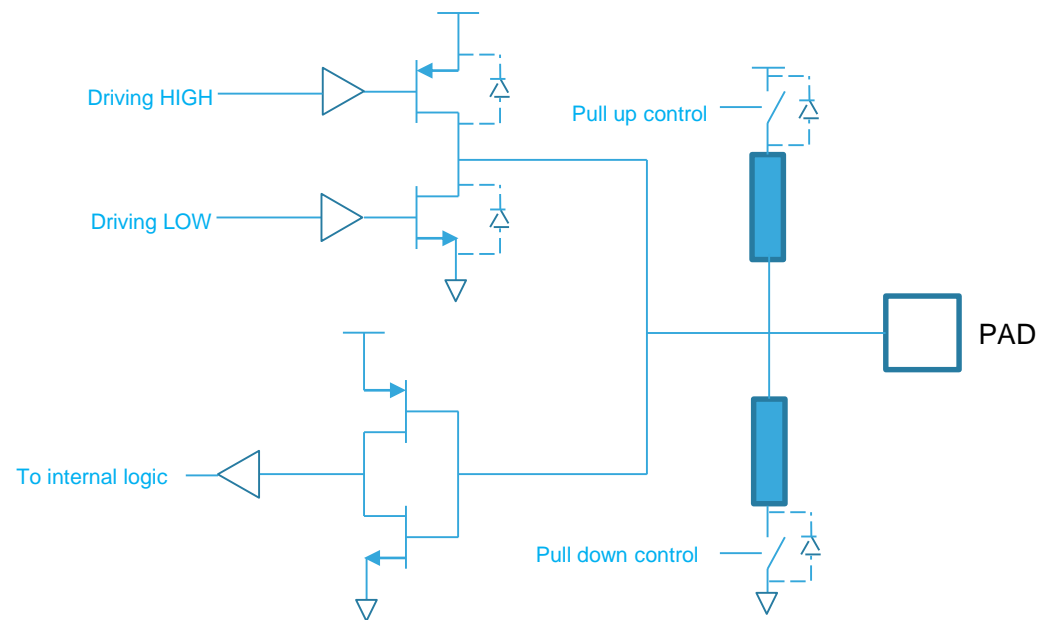- The circuit is made with 3.3V technology transistors, which can accept up to 3.6V.
 - There is parasitic diode from PAD to VDD, GND to PAD. Pad voltage must be put in the $-0.3V$ to the $VDD + 0.3V$ (where parasitic diode does not become forward biased).




IO equivalent circuit



5V tolerant CMOS IO structure

- Thanks to the voltage limiter, even 5V is applied to pad, transistor does not get 5V directly to the input stage.
- For the output stage, cascoded transistor technique is used such that off transistor does not get the more than 3.6V on each terminal (gate/source/drain)

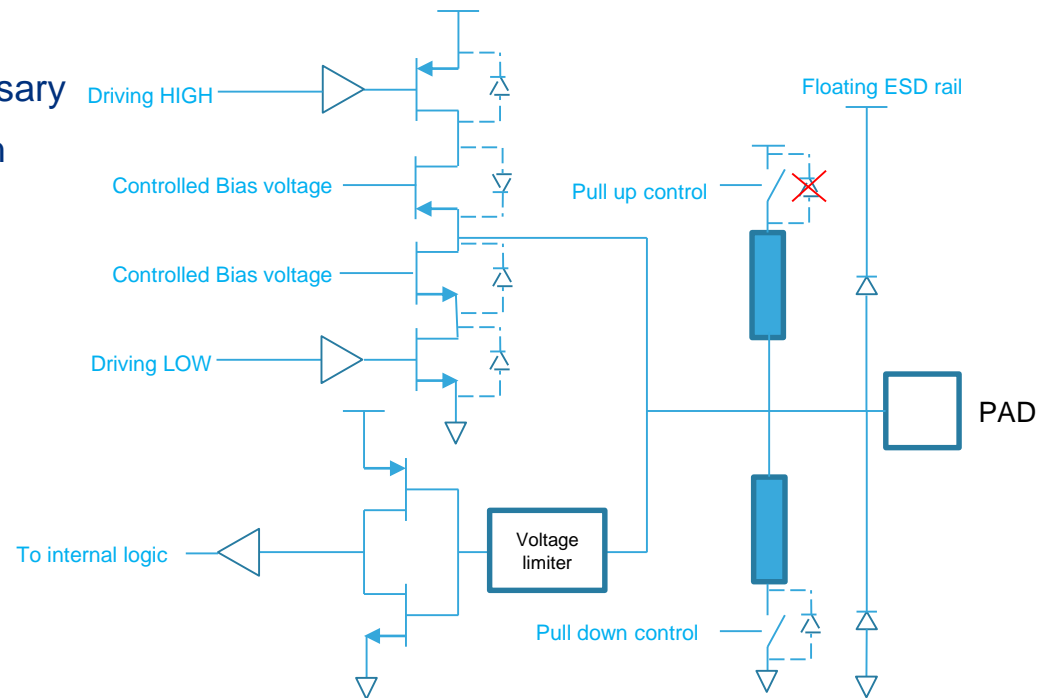- For the bias generation VDD is necessary
- Pull up switch also use isolated switch



5V IO equivalent circuit



5V tolerant

5

- In reality there are VDD+3.6V tolerant.
 - The pad can accept VDD+3.6V without introducing pad leakage (in general <1uA @125°C)
 - When VDD is not connected, (internal bias circuit disabled), only accept 3.6V.
- When Output buffer is enabled, it is not any more 5V tolerant
 - When PAD is 5V, then IO drives high, it will create simply short circuit between 5V to VDD.
 - When PAD is 5V, then IO drives low, it will create simply short circuit between 5V to GND.
- When Open drain with external pull up 5V is used
 - Hi-Z behaves High output, external pull up will define the output voltage (5V). (No problem)
 - Low means driving low. Thanks to pull up resistor with voltage drop, when NMOS is enabled, output PAD become low (0V).




5V tolerant

6


- Input threshold voltage is CMOS level
 - $V_{IH} \approx 2/3 V_{DD}$
 - $V_{IL} \approx 1/3 V_{DD}$
 - The voltage higher than V_{DD} is simply translated as high level

Application example : I2C

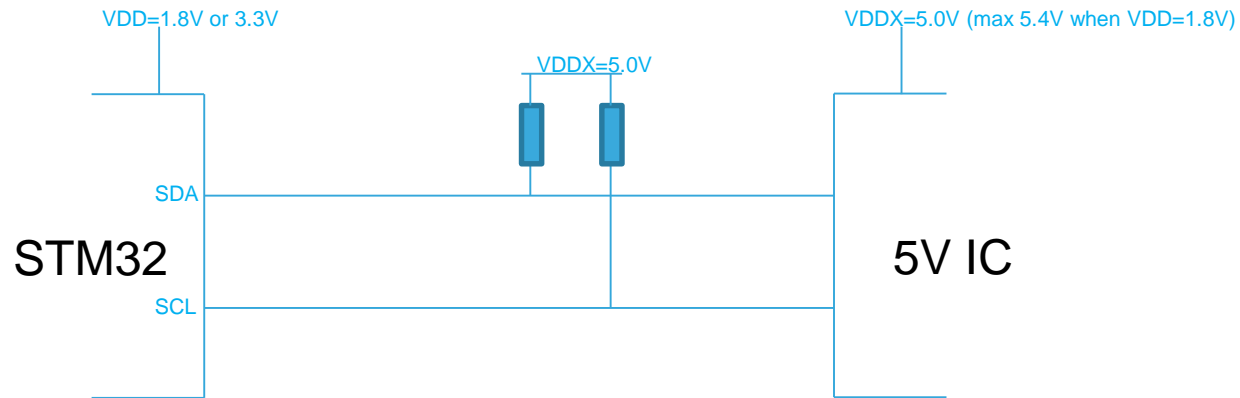- STM32 supplied by 1.8V or 3.3V can directly communicate with 5V I2C bus.





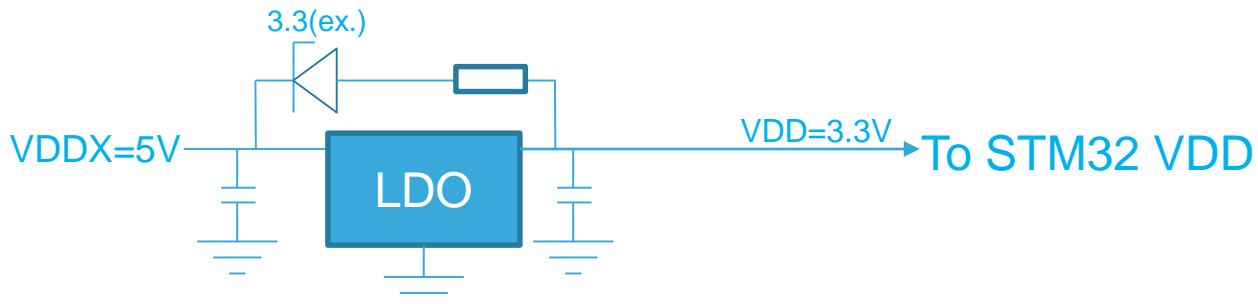- If there is condition when VDD=0V, VDDX=5V (even it is transient), it is recommended to place the zenner diode (ex. 3.3V) between VDD and VDDX.
 - For example VDD is output of LDO supplied by VDDX




Application example : USB VBUS

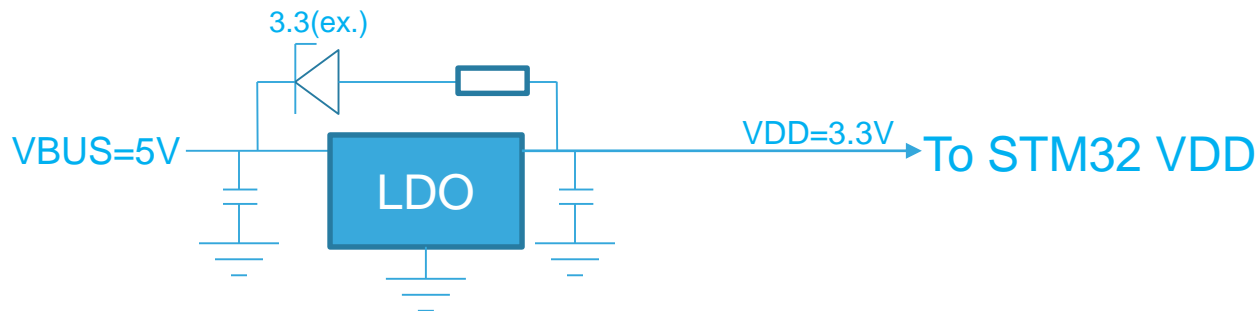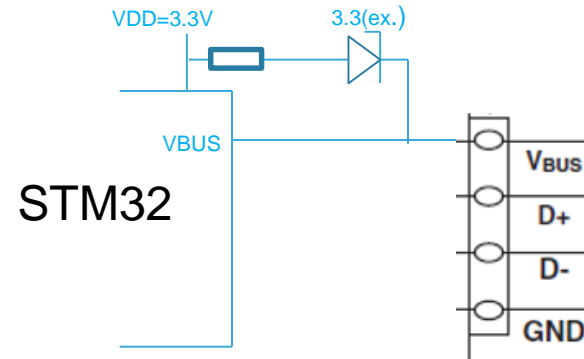- VBUS pad of STM32 is 5V tolerant.
 - However it needs to respect the VDD+3.6V absolute maximum ratings
- If STM32 supply is from independent supply.
 - It is not allowed to connect VBUS when STM32 is not supplied.
 - Or place the zenner diode (ex.3.3V) between VBUS and VDD
- If STM32 supply is from LDO supplied by VBUS
 - It is recommended to have zenner diode(ex. 3.3V)



Application example : Triac Drive

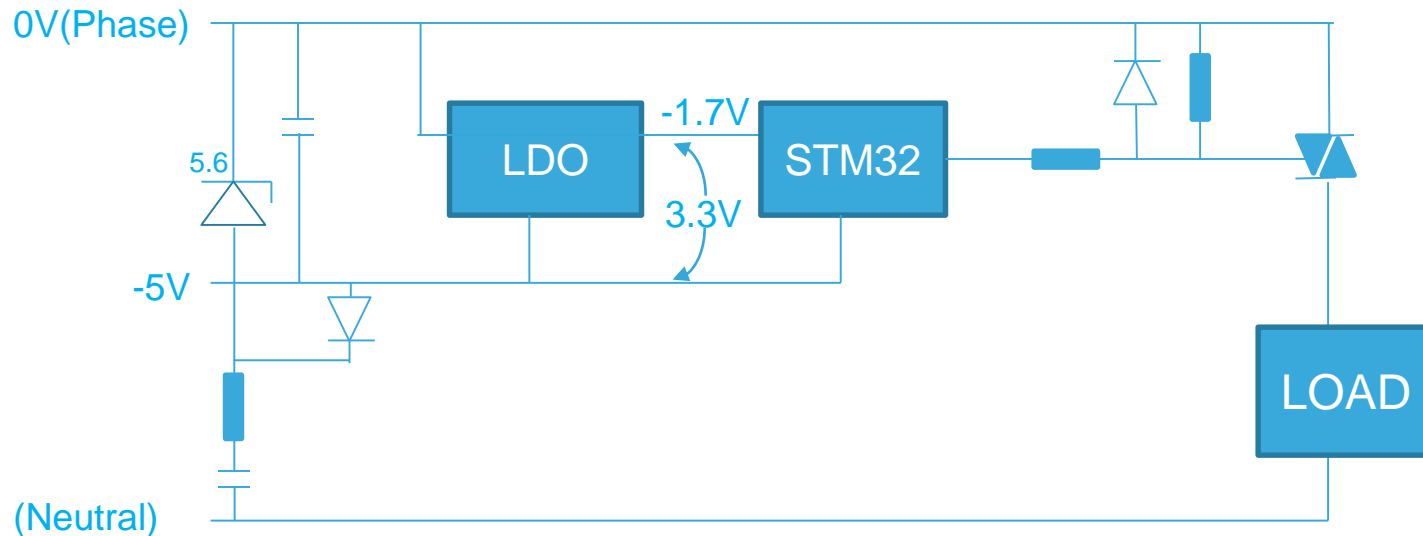
- This example is shown for the -5V supply system



- STM32 GPIO need to be set up as Open-drain mode
 - If IO drive current is not enough, coupled of GPIO can be paralleled.

Application example : White LED Drive

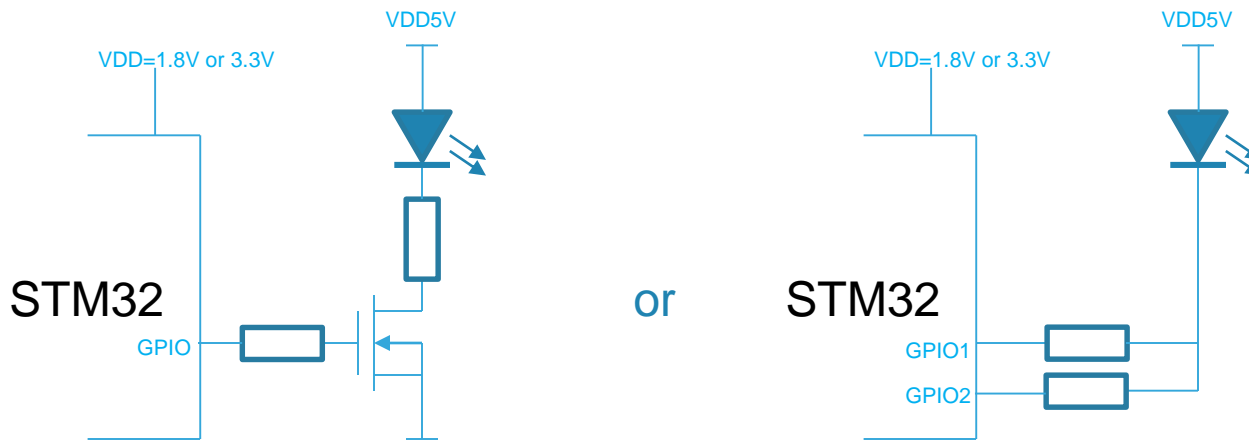
- White LED need typical ~20mA of the current with Vf of 3.5V(typ) 4V(max)
 - As STM32 maximum sink current is 25mA, it is not enough margin to drive direct
 - Use External MOSFET(or BJT) or Drive by two GPIO can be the option.



- For the GPIO parallel drive, open drain mode must be used.
 - The Ground current will be huge compare to the MCU consumption. GND layout need to be attentioned.

Application example : UART

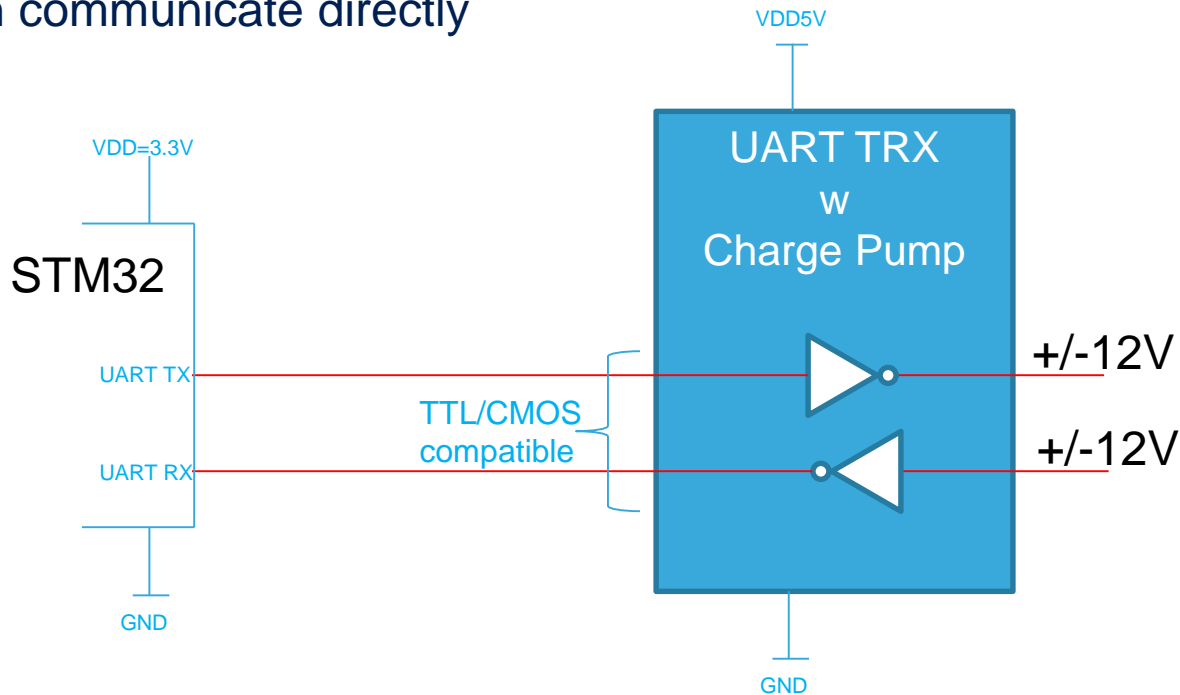
- If UART transceiver to communicate is 5V supply with TTL compatible, STM32 can communicate directly



- If 5V UART interface input is TTL compatible, $V_{OI} < 0.8V$, $V_{OH} > 2.0V$ so 3.3V CMOS output can drive without problem
- STM32 FT pad can accept 0 to 5V CMOS level input when VDD=3.3V.

IO usage for the 5V ADC connection

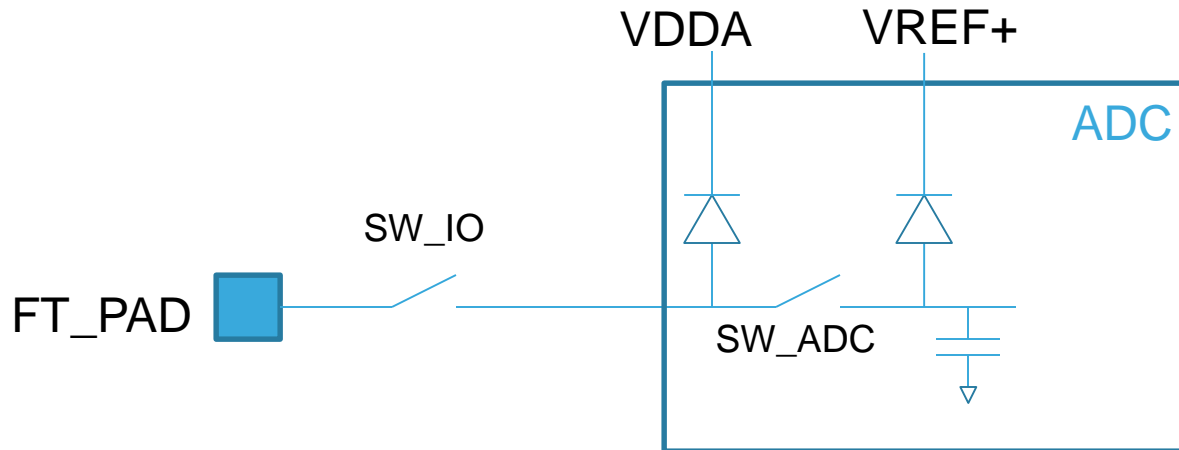
- STM32 has FT (5V tolerant) pads which connected to the ADC input.
- When ADC is not connected (analog switch in IO is not closed), IO can accept VDD+3.6V. So 5V apply to FT pad can be granted.
- However once IO input is connected to the ADC, and during the sampling phase, parasitic diode to VDDA and/or VREF+ will be forward biased.



- It is recommended to clamp the input voltage with external clamp (e.g. series resistor and the schottky diode to VREF+ voltage level)

IO usage for the 5V ADC connection

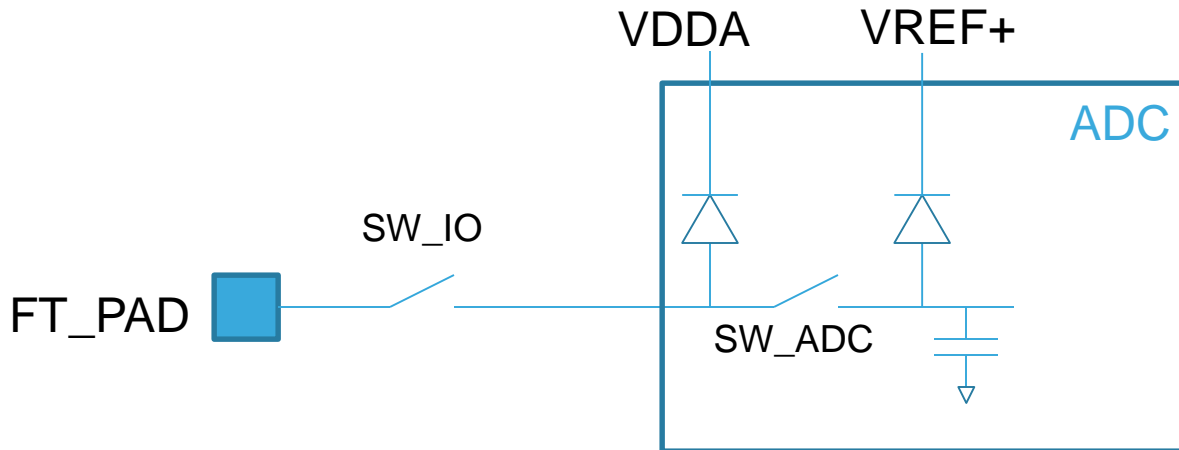
- STM32 has FT (5V tolerant) pads which connected to the ADC input.
- When ADC is not connected (analog switch in IO is not closed), IO can accept VDD+3.6V. So 5V apply to FT pad can be granted.
- However once IO input is connected to the ADC, and during the sampling phase, parasitic diode to VDDA and/or VREF+ will be forward biased.



- It is recommended to clamp the input voltage with external clamp (e.g. series resistor and the schottky diode to VREF+ voltage level)

Work around proposal

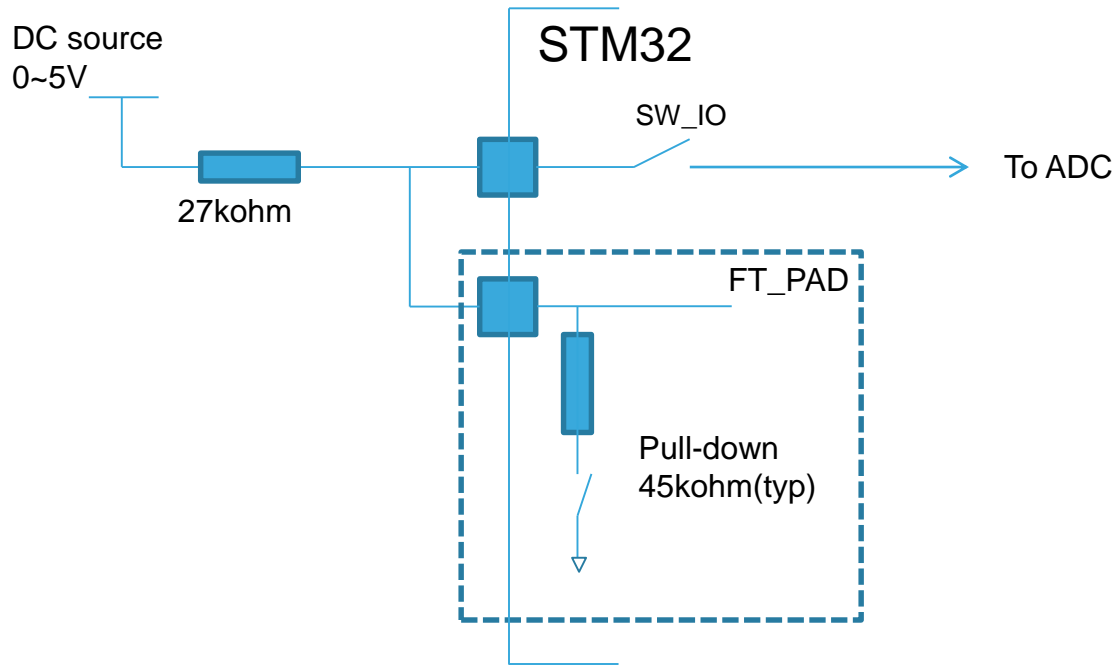- If there is unused FT pad available on STM32, connect this IO to the ADC input pad with parallel configuration.



1. The ADC will make conversion with other FT_PAD pull-down enabled
 2. If first ADC conversion result is less than 2V(which indicated the DC source is inside the ADC input range), ADC will re-do the conversion with pull-down disabled.
- Above method avoid the parasitic diode forward bias.